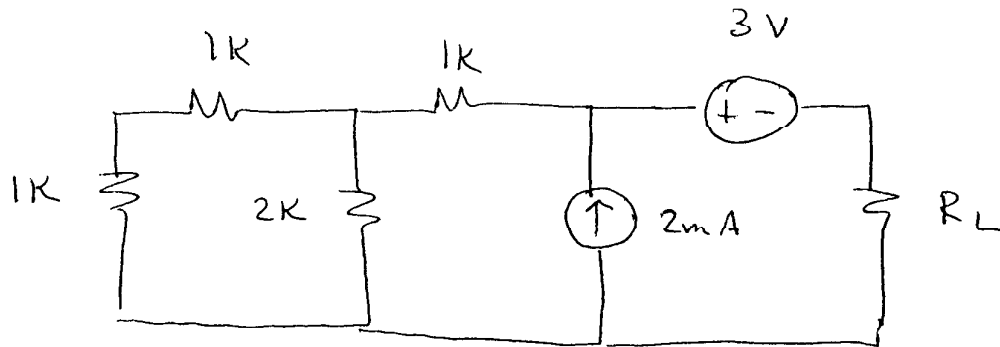


ECE 210 Q6 F'00 10/17/00

NAME: KEY

Honor Code:


Find the thevenin equivalent for the following circuit.



$$R_{TH} = 2000 \Omega$$

$$V_{TH} = 1V$$

$V_{oc}$ : use circuit simplification

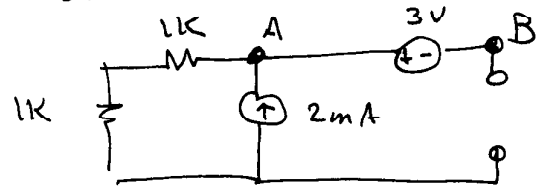

$$\frac{A}{2} - 2 = 0 \quad \underline{A = 4V}$$

$$B - A = 3 \quad \underline{B = 1V}$$


$$\underline{V_{oc} = 1V}$$

$R_{TH}$ :

1K & 1K in series



2K & 2K in parallel

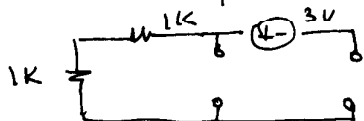

$$\underline{R_{TH} = 2K}$$